


Topic 3

Methods for precision measurement of dc current and dc voltage.

Modern potentiometers.

Measurement of voltage, power and energy in audio-frequency range.

Current balance

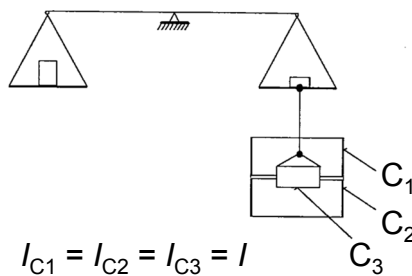


I_{C_1} enters C_1 at the bottom and leaves it at the top,

I_{C_2} enters C_2 at the top and leaves it at the bottom. \Rightarrow

\Rightarrow Electromagnetic forces on the suspended coil, produced by these two currents, are of the same sense.

Current balance

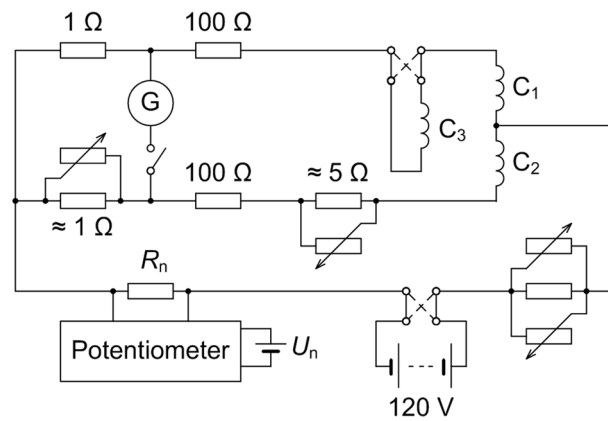

Current balance

$$F_{13} = I_{C1} I_{C3} \frac{\partial M_{13}}{\partial z} = I^2 f_{13}$$

$$M_{13} = \frac{\mu \mu_0}{4\pi} \iint_{C_1, C_3} \frac{d\sigma_1 d\sigma_3}{a_{13}}$$

(Neumann's formula)

Current balance

$$F_{23} = I_{C2} I_{C3} \frac{\partial M_{23}}{\partial z} = I^2 f_{23}$$

From symmetry,

$$f_{13} = f_{23} = f$$

Resulting electromagnetic force on C_3 is

$$F = F_{13} + F_{23} = 2fI^2$$

Current balance operation

- The mass of the suspended coil plus the vertical electromagnetic force exerted on it are counterbalanced by means of a mass m on the left scale pan.
- After reversing the current in the suspended coil, the change Δm of this mass, necessary to offset the change ΔF of the acting electromagnetic force, is determined.

$$\Delta F = 4fI^2 = \Delta m \cdot g \Rightarrow I = \frac{1}{2} \sqrt{\frac{\Delta m \cdot g}{f}}$$

Current balance operation

- A separate moving experiment makes it possible to avoid the troublesome calculation of f from the dimensions of the coils:

Coil C_3 , which is threaded by the magnetic flux produced by the current I flowing in C_1 and C_2 , is moved with a constant velocity v in the vertical direction, a voltage $u(t)$ being induced in it:

$$u(t) = 2I \frac{\partial M_{13}}{\partial t} = 2I \frac{\partial M_{13}}{\partial z} \frac{\partial z}{\partial t} = 2Iv \frac{\partial M_{13}}{\partial z}$$

Current balance operation

- If a voltage drop $U = RI$ is produced by the current I on a known resistance R and if a velocity v is chosen for which

$$u(t) = U$$

- in the moment of passage of the scale beam through its equilibrium position,

$$f = \frac{\partial M_{13}}{\partial z} = \frac{R}{2v}$$

Electronic kilogram


- In case that quantum standards of voltage and resistance are used to measure the current I flowing in the coils in course of the weighing experiment, a current balance with a known value of f can be used to produce known values of electromagnetic force and to monitor variations of masses which are used to counterbalance it.

Voltage balance


- is an apparatus based on counterbalancing the attractive force between electrodes of a capacitor.

$$F_z = \frac{1}{2} U^2 \frac{\partial C}{\partial z}$$


DC comparator potentiometer

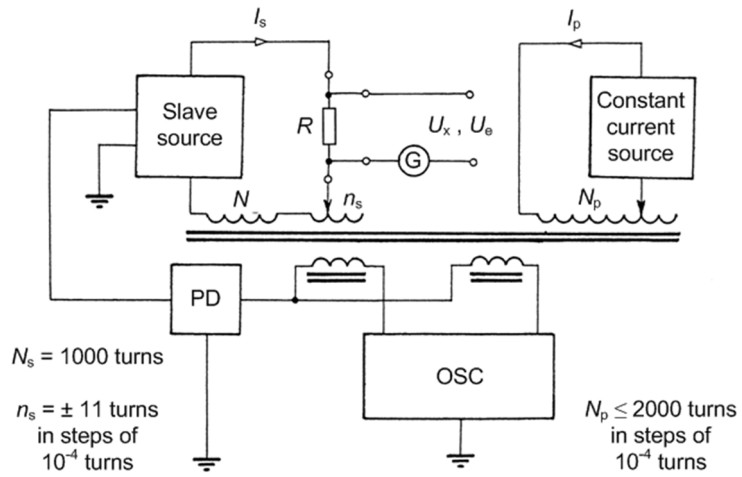

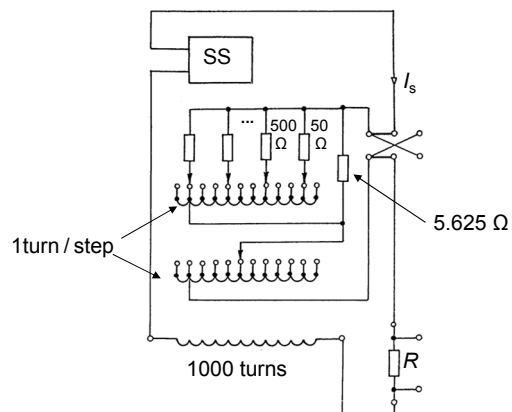Realization of the equivalent of fractional turns



Josephson potentiometer

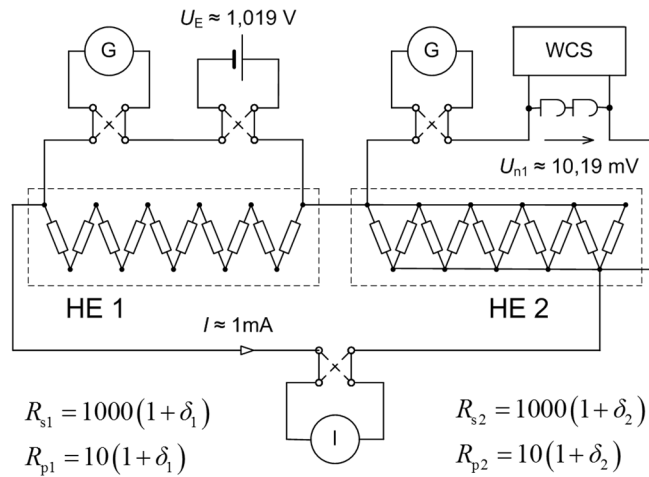

With Hamon standards interchanged


$$\frac{U_E}{R_{s2}} = \frac{U_{n2}}{R_{p1}}$$

$$\frac{U_E}{R_{s1}} = \frac{U_{n1}}{R_{p2}}$$

$$\begin{aligned}
 U_{n1} + U_{n2} &= U_E \left(\frac{R_{p2}}{R_{s1}} + \frac{R_{p1}}{R_{s2}} \right) = 0,01 U_E \left(\frac{1 + \delta_2}{1 + \delta_1} + \frac{1 + \delta_1}{1 + \delta_2} \right) = \\
 &= 0,01 U_E \frac{(1 + \delta_2)^2 + (1 + \delta_1)^2}{(1 + \delta_1)(1 + \delta_2)} = 0,01 U_E \frac{1 + 2\delta_2 + \delta_2^2 + 1 + 2\delta_1 + \delta_1^2}{1 + \delta_1 + \delta_2 + \delta_1\delta_2} \doteq \\
 &\doteq 0,01 U_E \frac{2 + 2\delta_1 + 2\delta_2}{1 + \delta_1 + \delta_2} = 0,02 U_E
 \end{aligned}$$

$$U_E = 50(U_{n1} + U_{n2})$$

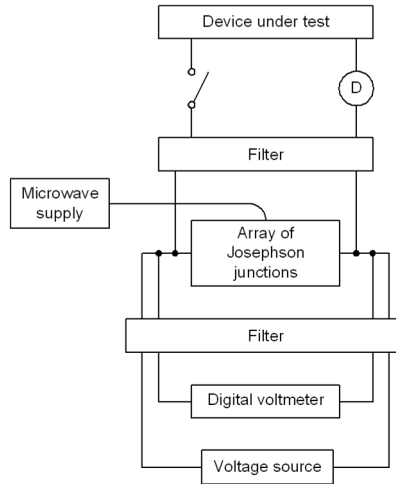Calibration of an electronic voltage standard




Primary voltage standard system with closed-cycle refrigerator




Primary voltage standard system with closed-cycle refrigerator

- 100 nV calibration accuracy
- -11 V to 11 V range available from 10-V system
- typically 1 hour stability time at 10 V for 10-V system
- automatic voltage calibration in minutes
- automatic calibration of DVMs
- complete system diagnostics


RMS/DC thermocouple comparator

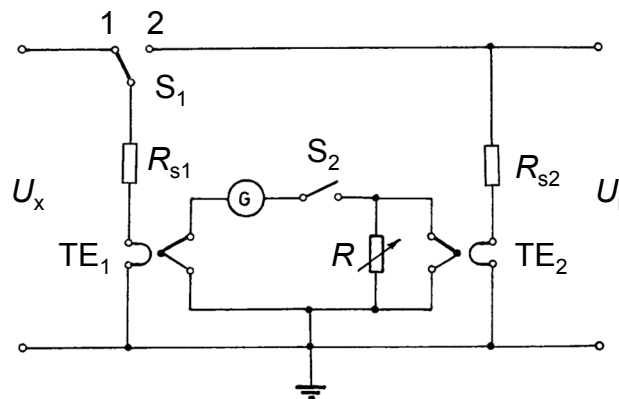


Automatic RMS/DC thermocouple comparator

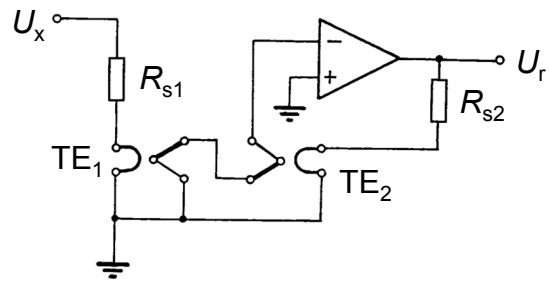


Thermocouple protection

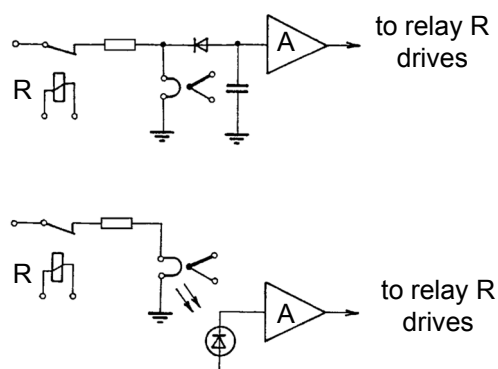

RMS/DC thermistor comparator

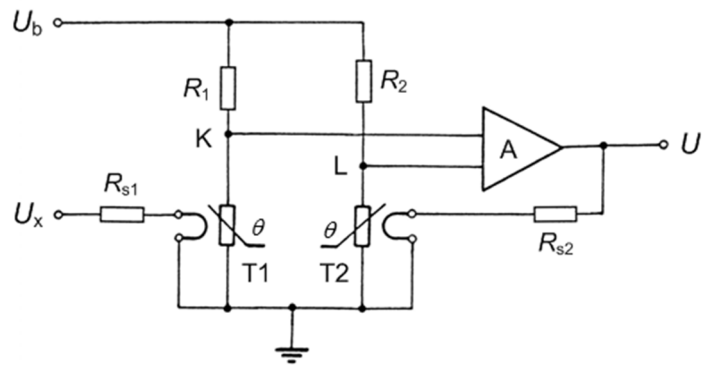

Improved RMS/DC thermistor comparator

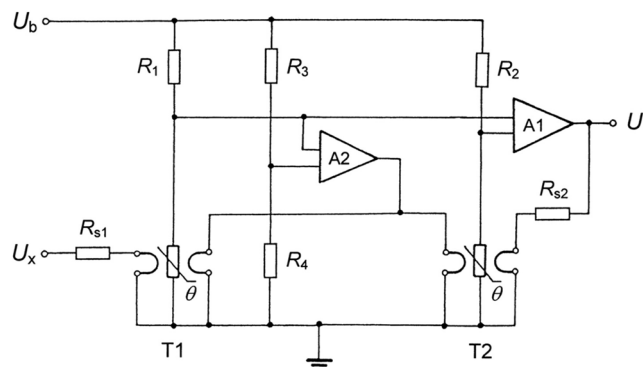

Definitions for powers

Sinusoidal voltages and currents

Active power : $P = U I \cos \varphi$

Apparent power : $S = U I$

Reactive power : $Q = U I \sin \varphi$

$$S^2 = P^2 + Q^2$$

Definitions for powers

Nonsinusoidal voltages and currents

$$U = \sqrt{\sum_{n=1}^{\infty} U_n^2} \quad \text{and} \quad I = \sqrt{\sum_{n=1}^{\infty} I_n^2}$$

Apparent power : $S = U I$

Active power : $P = \sum_{n=1}^{\infty} U_n I_n \cos \varphi_n$

Reactive power : a number of different definitions have been proposed

Definitions for powers

Budeanu's definition for reactive power :

$$Q_B = \sum_{n=1}^{\infty} U_n I_n \sin \varphi_n$$

$$S^2 = P^2 + Q_B^2 + D_B^2$$

Distortion power :

$$D_B = \sqrt{S^2 - P^2 - Q_B^2}$$

Practical definitions for powers proposed by the IEEE Working Group

on Nonsinusoidal Situations

$$U^2 = U_1^2 + U_H^2 = U_1^2 + \sum_{n \neq 1} U_n^2$$

$$I^2 = I_1^2 + I_H^2 = I_1^2 + \sum_{n \neq 1} I_n^2$$

$$(UI)^2 = (U_1 I_1)^2 + (U_1 I_H)^2 + (U_H I_1)^2 + (U_H I_H)^2$$

Practical definitions for powers proposed by the IEEE Working Group

Fundamental apparent power :


$$\begin{aligned}(U_1 I_1)^2 &= S_1^2 = P_1^2 + Q_1^2 = \\ &= (U_1 I_1 \cos \phi_1)^2 + (U_1 I_1 \sin \phi_1)^2\end{aligned}$$

Non-fundamental apparent power :

$$S_N^2 = (U_1 I_H)^2 + (U_H I_1)^2 + (U_H I_H)^2 = S^2 - S_1^2$$

$$\text{Nonactive power : } N^2 = S^2 - P^2$$

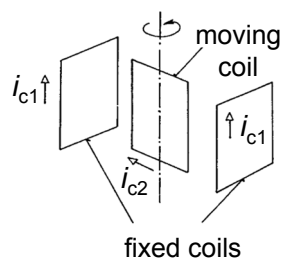Electrodynamic method of measurement of AC power



$$\text{Inst. torque} = i_{c1} i_{c2} \frac{dM}{d\alpha}$$


$$\text{mean torque} = \langle i_{c1} i_{c2} \rangle \frac{dM}{d\alpha}$$

$$\langle i_{c1} i_{c2} \rangle = \frac{1}{T} \int_0^T i_{c1} i_{c2} dt$$


$$\begin{aligned}i_{c1} &= i_1 + I_1 \\ i_{c2} &= i_2 - I_2\end{aligned}$$

$$\langle i_1 i_2 \rangle = I_1 I_2 \Rightarrow \text{mean torque} = 0 \Rightarrow \alpha = 0$$

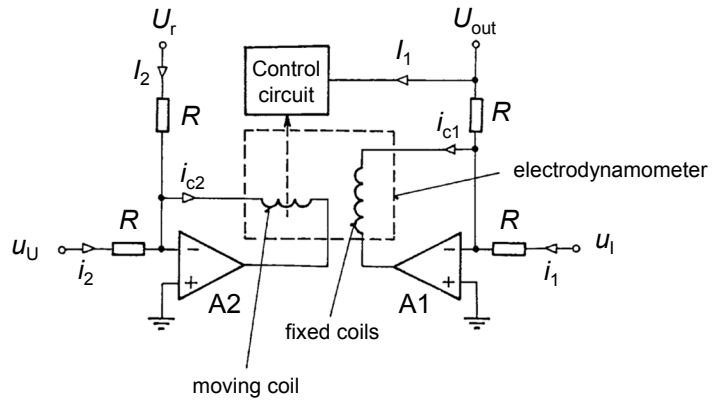Electrodynamic method of measurement of AC power



Thermal wattmeter

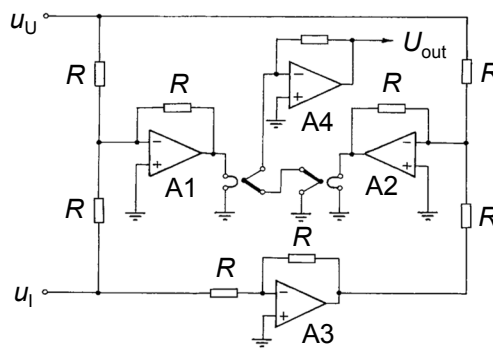

$$U_{out} = k \langle (u_U + u_I)^2 - (u_U - u_I)^2 \rangle = 4k \langle u_U u_I \rangle$$

Digital sampling method

$$P = \frac{1}{T} \int_0^T u(t)i(t)dt = \frac{1}{T} \int_0^T p(t)dt$$
$$p(t) = P + \sum_{k=1}^{\infty} P_k \sin\left(2\pi k \frac{t}{T} + \varphi_k\right)$$
$$\hat{P} = \frac{1}{n} \sum_{l=0}^{n-1} u(t_l) i(t_l) = \frac{1}{n} \sum_{l=0}^{n-1} p(t_l)$$
$$|\Delta P| = \left| \hat{P} - P \right| \leq \sum_{k>0}^* P_k$$

The starred summation is over only those power harmonics whose frequencies are integer multiples of the sampling frequency.