

Topic 4

Bridges for dc and ac measurements of resistance.

Transformer and current-comparator-based capacitance bridges.

Bridges for dc and ac measurements of resistance


- Need to cover measurement range from $10 \mu\Omega$ up to $10 \text{ P}\Omega$



NIST, Fluke,
MINTL, Ceasbuild


- Measurement methods – ratio between known and unknown standard:
 - Potentiometric method - apply same I , measure ratio of V
(for medium and high-ohm resistances)
 - Comparator method - apply same U , measure ratio of I
(for low-ohm and medium resistances)

Kelvin double bridge

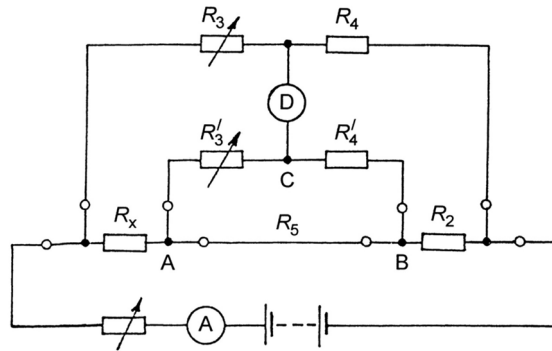

$$R_x = R_2 \frac{R_3}{R_4} + R_5 \frac{R_4}{R_3 + R_4 + R_5} \left(\frac{R_3}{R_4} - \frac{R_3}{R_4} \right)$$

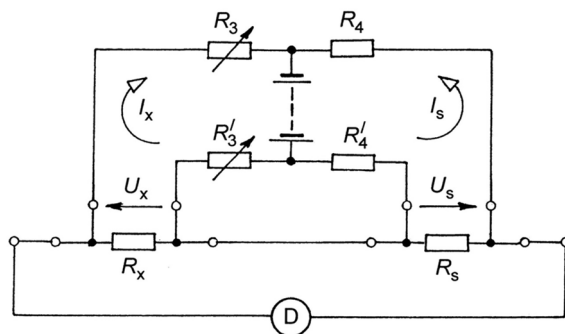Kelvin double bridge with source and detector interchanged




$$U_x = U_s$$

$$R_x I_x = R_s I_s$$

$$\frac{R_x}{R_s} = \frac{I_s}{I_x}$$

DC comparator bridge

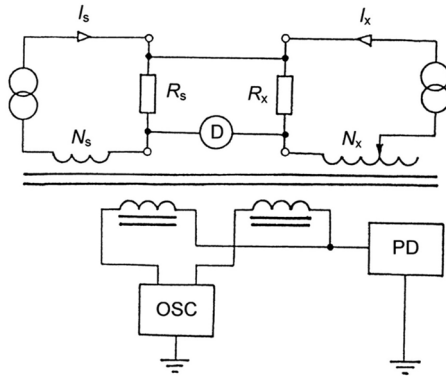


$$R_x I_x = R_s I_s$$

$$N_x I_x = N_s I_s$$

$$R_x = \frac{N_x}{N_s} R_s$$

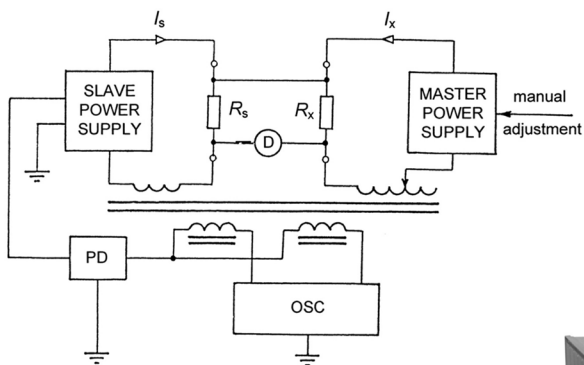Bridge based on an automatically balanced DC comparator




$$R_x = \frac{N_x}{N_s} R_s$$



Coaxial ac bridges

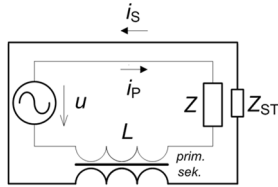- All components are surrounded by electrical shields
- All components are connected by coaxial cables
- Goal: currents in the outer shields are equal to opposite of currents in the inner components and conductors
- Coaxial bridge – two superposed networks:




$$\frac{d(\Phi_p - \Phi_s)}{dt} = L \frac{d(i_p - i_s)}{dt} = j\omega L(i_p - i_s) = i_s Z_{ST}$$

$$i_s = \frac{i_p}{1 + \frac{Z_{ST}}{j\omega L}}$$

$$Z_{ST} \ll \omega L \rightarrow i_s \approx i_p$$

- The ideal coaxial bridge produces no external magnetic field and zero electric field → the bridge is insensitive to external fields



AC transformer C-C bridge

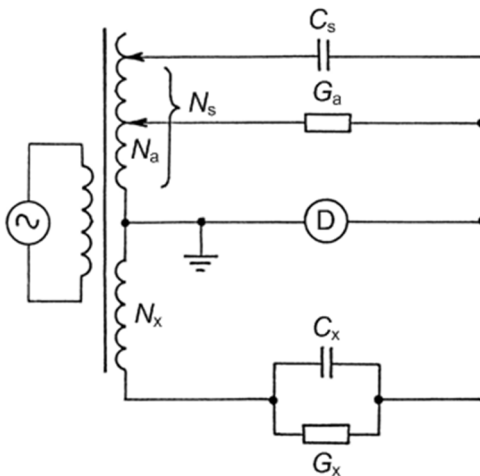


$$C_x = \frac{N_s}{N_x} C_s$$

$$G_x = \frac{N_a}{N_x} G_a$$


AC comparator C-C bridge

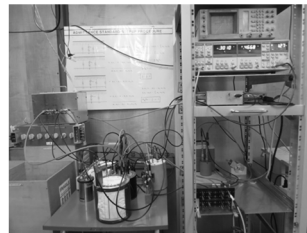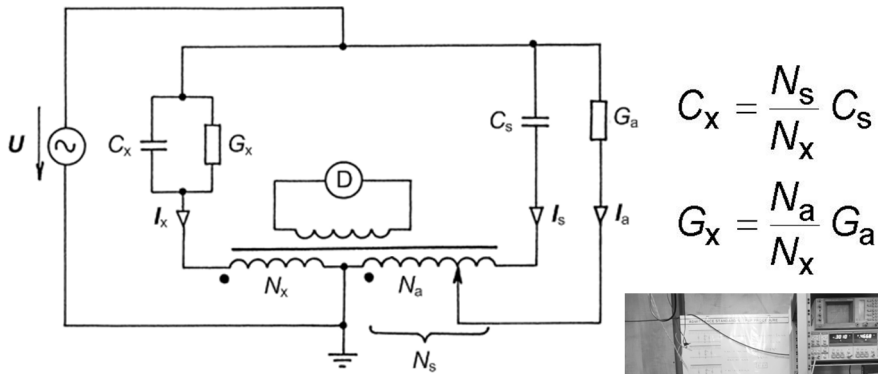

High voltage comparator C-C bridge

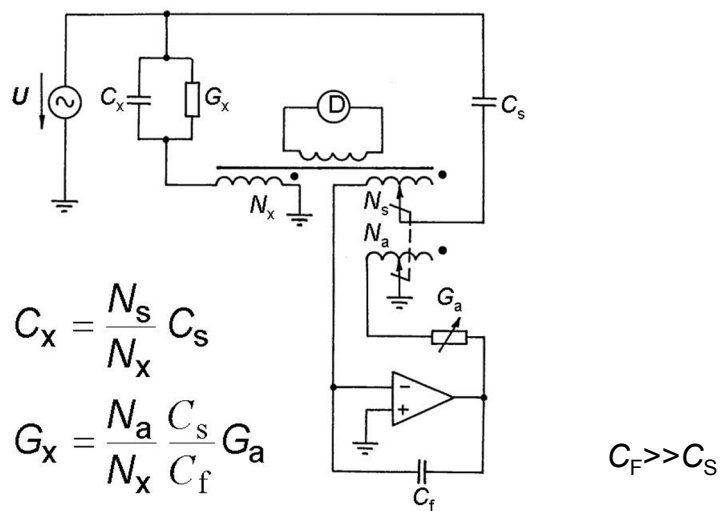

Shielding of AC comparator C-C bridge

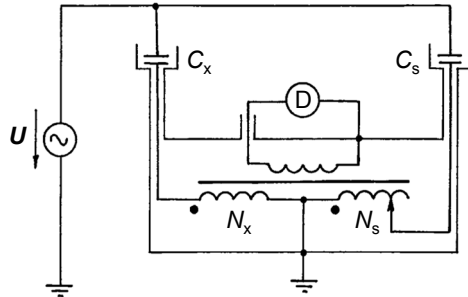


- Omitting effects of parasitic capacitances


Development of a four-terminal-pair C-C bridge

Development
of a four-terminal-pair
C-C bridge

Simple C-C bridge

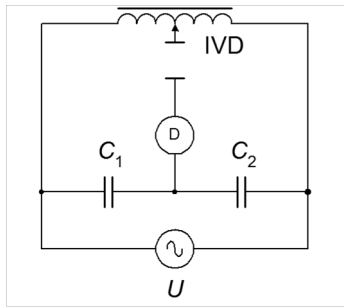


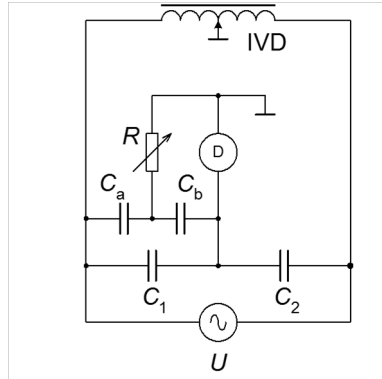Simple bridge for comparing
2TP lossless capacitors




Simple bridge for comparing
2TP capacitors with losses


Injection and combining network

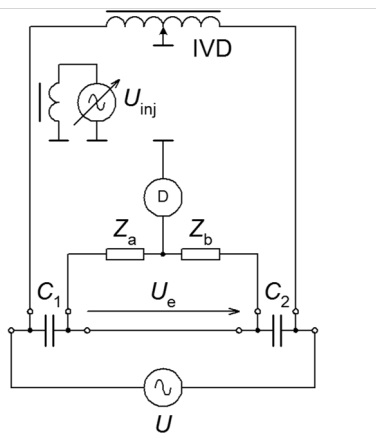

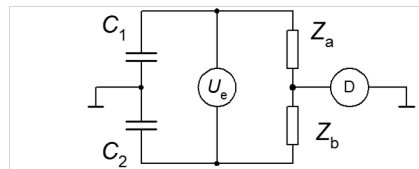Bridge for comparison of 4TP lossless
capacitors




Improved version

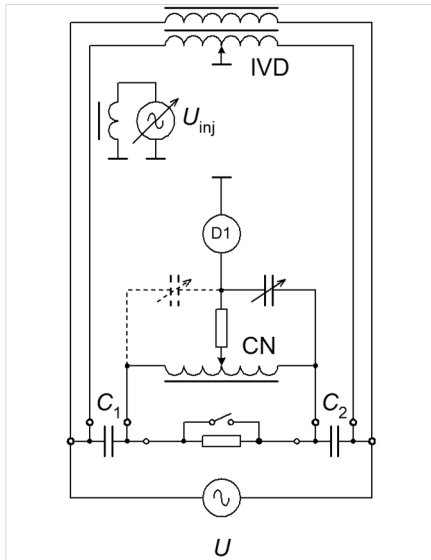

- Improving accuracy with:
- Two-stage divider
 - CN formed with variable IVD

Four-terminal pair R-R bridge


R-R bridge, version 1

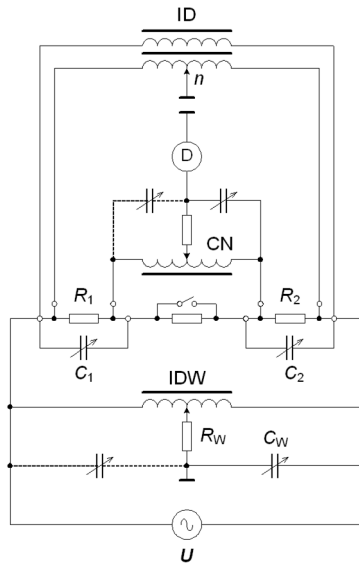

- Two stage IVDs
- Compensation networks
- Wagner earth circuit


- Measurement of time constant difference between R_1 and R_2 : small variable capacitors C_1, C_2

R-R bridge, version 2

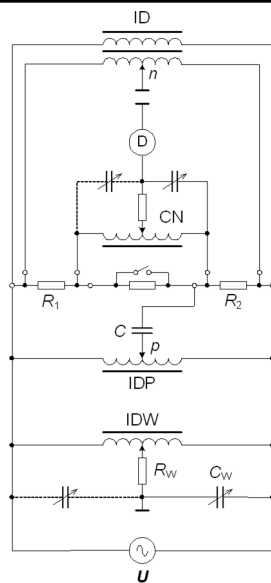

- Quadrature balance performed with IDP and C

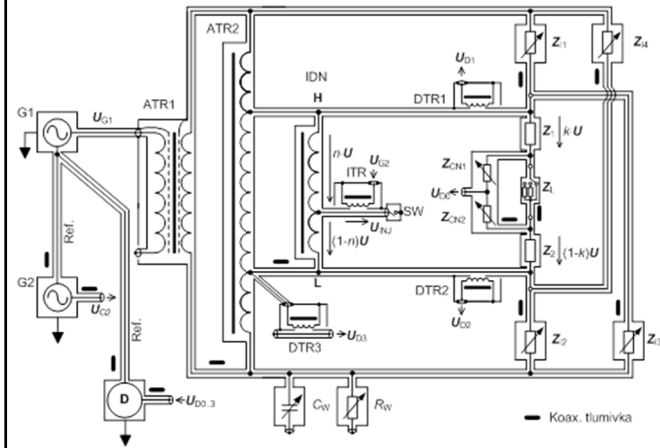Example of realization of a fully coaxial R-R bridge



$$k_i = n + \frac{U_{DNR}}{U}$$

$$K_i = \frac{k_i}{1 - k_i}$$

$$K = \sum_{i=1}^N K_i$$

